

Digital Circuit, Logic, Boolean Algebra, and Truth Table


교재 2장 1절 ~ 5절

Switches

■ Electronic switches are the basis of binary digital circuits

➤ Electrical terminology

 - **Voltage:** Difference in electric potential between two points (volts, V)
 - Analogous to water pressure
- **Resistance:** Tendency of wire to resist current flow (ohms, Ω)
 - Analogous to water pipe diameter
- **Current:** Flow of charged particles (amps, A)
 - Analogous to water flow
- $V = I * R$ (Ohm's Law)
 - $9\text{ V} = I * 2\text{ ohms}$
 - $I = 4.5\text{ A}$



If a 9V potential difference is applied across a 2 ohm resistor, then 4.5 A of current will flow.



Switches

■ A switch has three parts

- Source input, and output
 - Current tries to flow from source input to output
- Control input
 - Voltage that controls whether that current can flow

■ The amazing shrinking switch

  
- 1930s: Relays
- 1940s: Vacuum tubes
- 1950s: Discrete transistor
- 1960s: Integrated circuits (ICs)
 - Initially just a few transistors on IC
 - Then tens, hundreds, thousands...









The CMOS Transistor

■ CMOS transistor

➤ Basic switch in modern ICs

 

      Silicon -- not quite a conductor or insulator:
Semiconductor




Boolean Logic Gates

Building Blocks for Digital Circuits

2.4

(Because Switches are Hard to Work With)

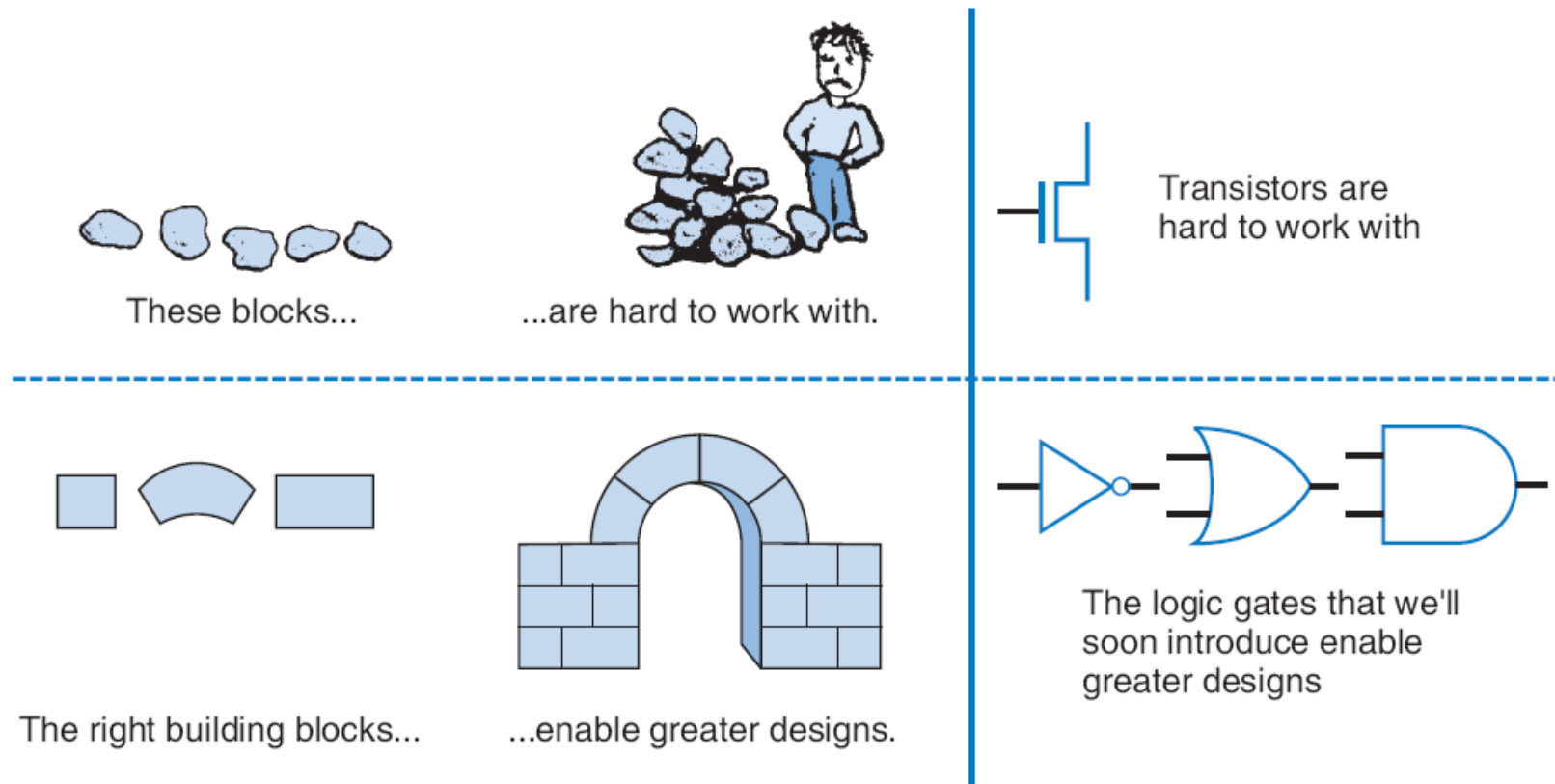

- “Logic gates” are better digital circuit building blocks than switches (transistors)
 - Why?...

Boolean Algebra and its Relation to Digital Circuits

- To understand the benefits of “logic gates” vs. switches, we should first understand Boolean algebra
- “Traditional” algebra
 - Variables represent real numbers (x, y)
 - Operators operate on variables, return real numbers ($2.5*x + y - 3$)
- *Boolean Algebra*
 - Variables represent 0 or 1 only
 - Operators return 0 or 1 only
 - Basic operators
 - AND: $a \text{ AND } b$ returns 1 only when both $a=1$ and $b=1$
 - OR: $a \text{ OR } b$ returns 1 if either (or both) $a=1$ or $b=1$
 - NOT: $\text{NOT } a$ returns the opposite of a (1 if $a=0$, 0 if $a=1$)

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0

Boolean Algebra and its Relation to Digital Circuits

- Developed mid-1800's by George Boole to formalize human thought

➤ Ex: "I'll go to lunch if Mary goes OR John goes, AND Sally does not go."

- Let F represent my going to lunch (1 means I go, 0 I don't go)
- Likewise, m for Mary going, j for John, and s for Sally
- Then $F = (m \text{ OR } j) \text{ AND NOT}(s)$

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1



➤ Nice features

- Formally evaluate
 - $m=1, j=0, s=1 \rightarrow F = (1 \text{ OR } 0) \text{ AND NOT}(1) = 1 \text{ AND } 0 = \underline{0}$
- Formally transform
 - $F = (m \text{ and NOT}(s)) \text{ OR } (j \text{ and NOT}(s))$
 - » Looks different, but same function
 - » We'll show transformation techniques soon
- Formally prove
 - Prove that if Sally goes to lunch ($s=1$), then I don't go ($F=0$)
 - $F = (m \text{ OR } j) \text{ AND NOT}(1) = (m \text{ OR } j) \text{ AND } 0 = 0$

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1


a	NOT
0	1
1	0

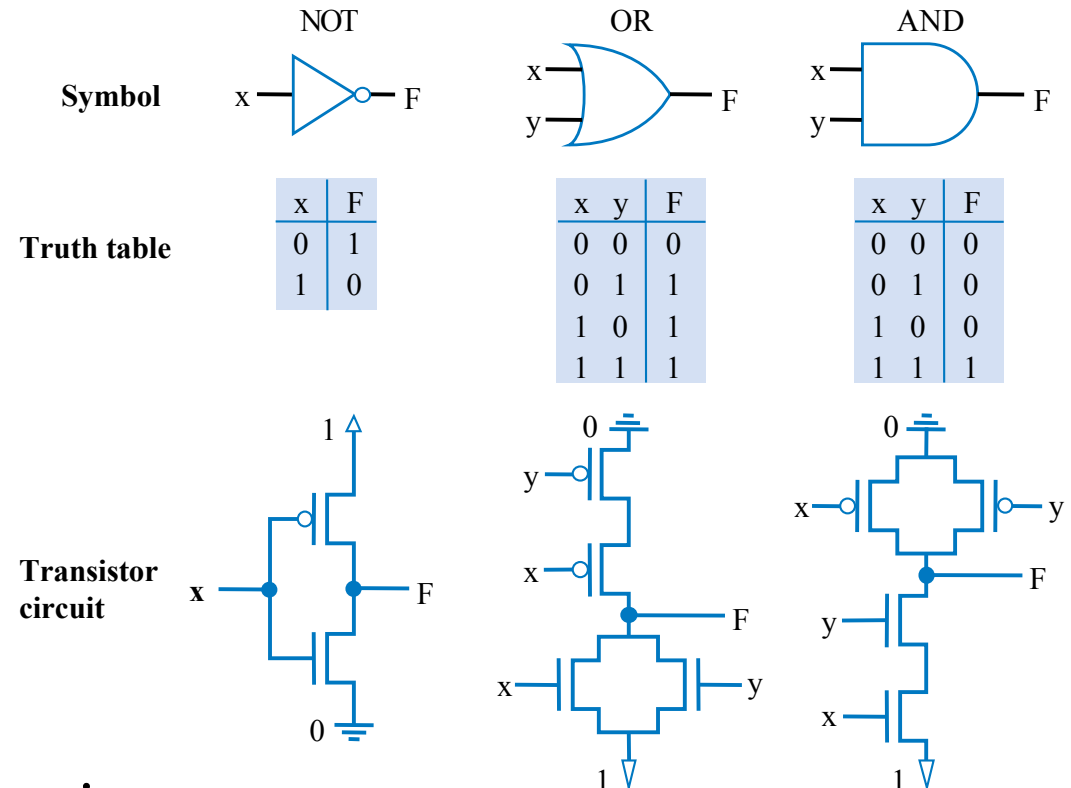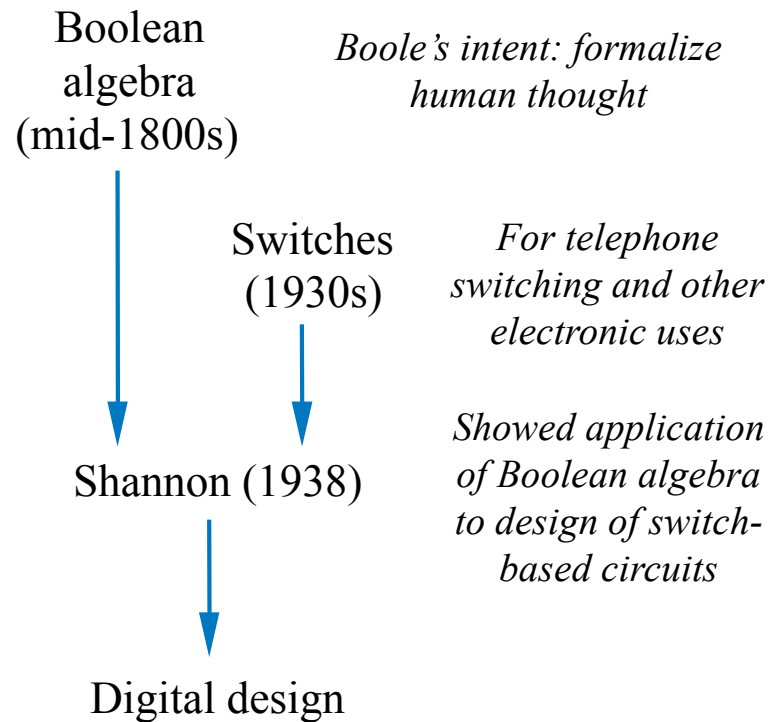Relating Boolean Algebra to Digital Design



■ Implement Boolean operators using transistors

 
- Call those implementations *logic gates*.
- Lets us build circuits by doing math –
– powerful concept





1 and 0 each actually corresponds to a voltage range

Next slides show how these circuits work.
Note: The above OR/AND implementations are inefficient; we'll show why, and show better ones, later.


NOT gate

 

x	F
0	1
1	0

  


When the input is 0


 


When the input is 1


OR gate

 

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

  


When an input is 1


 


When both inputs are 0


AND gate

 

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

  


When both inputs are 1

 

When an input is 0

Building Circuits Using Gates

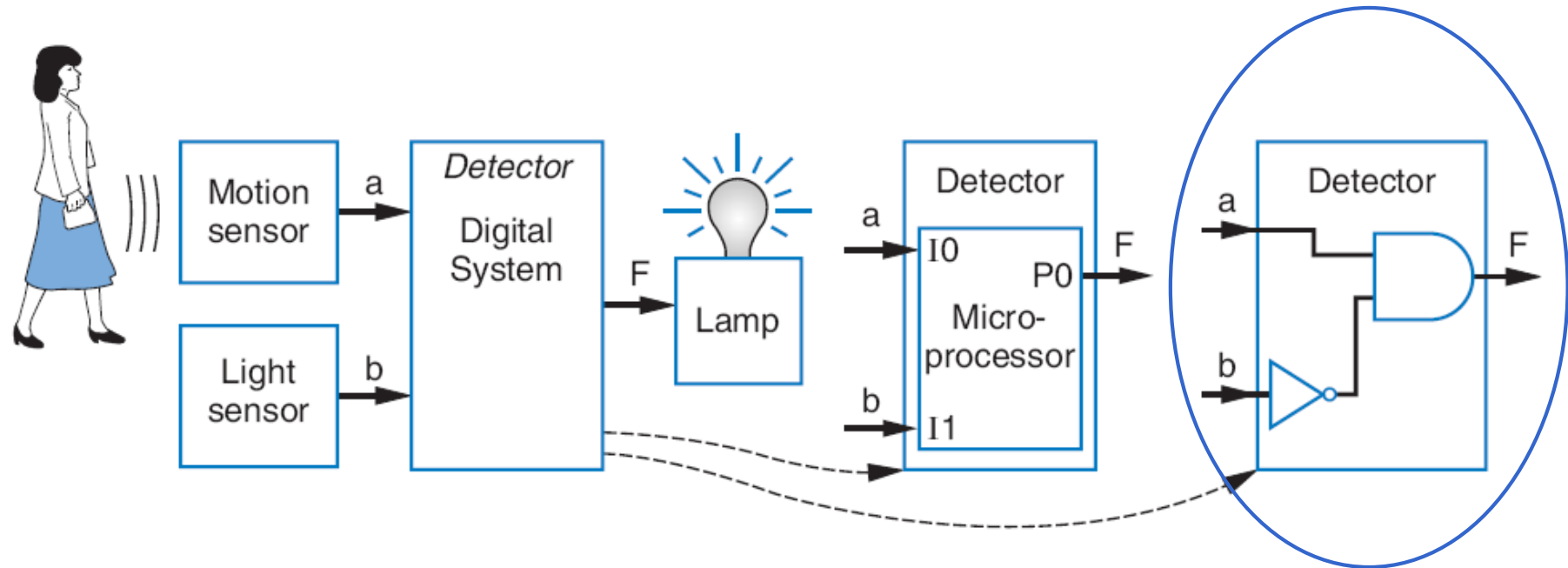


■ Recall Chapter 1 motion-in-dark example

- Turn on lamp ($F=1$) when motion sensed ($a=1$) and no light ($b=0$)
- $F = a \text{ AND NOT}(b)$
- Build using logic gates, AND and NOT, as shown
- We just built our first digital circuit!


 
Example: Converting a Boolean Equation to a Circuit of Logic Gates

Start from the output, work back towards the inputs

- Q: Convert the following equation to logic gates:
$$F = a \text{ AND NOT}(b \text{ OR NOT}(c))$$





More examples

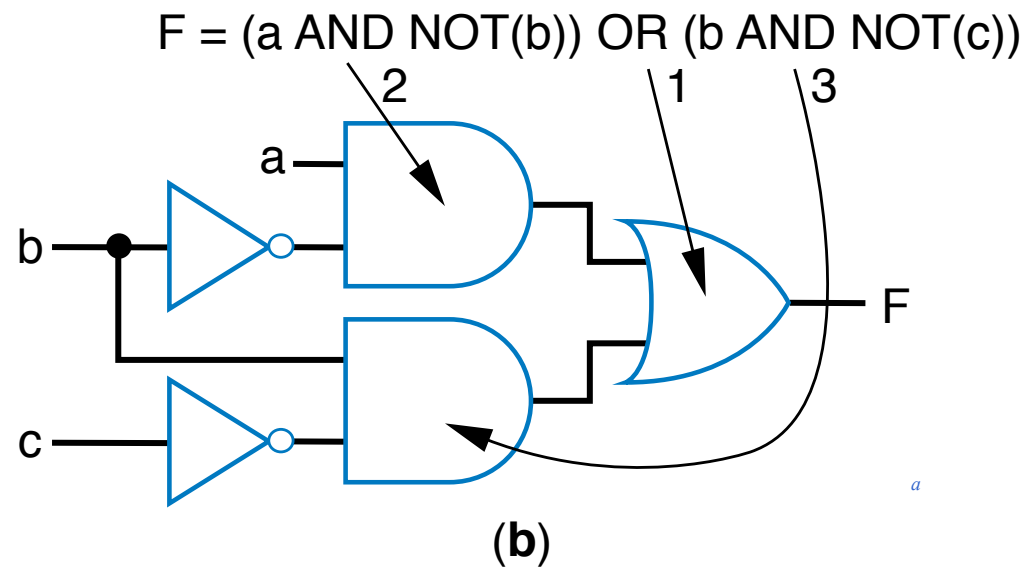 



Start from the output, work back towards the inputs

Using gates with more than 2 inputs

  


Can think of as $\text{AND}(a,b,c)$

  Some Gate-Based Circuit Drawing Conventions



a

 


a

 Example that Applies Boolean Algebra Properties


- Want automatic door opener circuit (e.g., for grocery store)

- Output: $f=1$ opens door
- Inputs:
 - $p=1$: person detected
 - $h=1$: switch forcing hold open
 - $c=1$: key forcing closed
- Want open door when
 - $h=1$ and $c=0$, or
 - $h=0$ and $p=1$ and $c=0$
- Equation: $f = hc' + h'pc'$



- Can the circuit be simplified?
 
$$\begin{aligned} f &= hc' + h'pc' \\ f &= c'h + c'h'p && \text{(by the commutative property)} \\ f &= c'(h + h'p) && \text{(by the first distrib. property)} \\ f &= c'((h+h')*(h+p)) && \text{(2nd distrib. prop.; tricky one)} \\ f &= c'((1)*(h+p)) && \text{(by the complement property)} \\ f &= c'(h+p) && \text{(by the identity property)} \end{aligned}$$




*Simplification of circuits is covered
in Sec. 2.11 / Sec 6.2.*

Boolean Algebra

- By defining logic gates based on Boolean algebra, we can *use algebraic methods to manipulate circuits*
 - Notation: Writing a AND b , a OR b , NOT(a) is cumbersome
 - Use symbols: $a * b$ (or just ab), $a + b$, and a'
 - Original: $w = (p \text{ AND NOT}(s) \text{ AND } k) \text{ OR } t$
 - New: $w = ps'k + t$
 - Spoken as “ w equals p and s prime and k , or t ”
 - Or just “ w equals p s prime k , or t ”
 - s' known as “complement of s ”
 - While symbols come from regular algebra, *don't* say “times” or “plus”
 - “product” and “sum” are OK and commonly used
- Boolean algebra precedence, highest precedence first.

Symbol	Name	Description
()	Parentheses	Evaluate expressions nested in parentheses first
'	NOT	Evaluate from left to right
*	AND	Evaluate from left to right
+	OR	Evaluate from left to right

 Example that Applies Boolean Algebra Properties




- Found inexpensive chip that computes:

- $f = c'hp + c'hp' + c'h'p$

- Can we use it for the door opener?

- Is it the same as $f = hc' + h'pc'$?

 

- Commutative

- $a + b = b + a$
 - $a * b = b * a$

- Distributive

- $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$

- Associative

- $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$

- Identity

- $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$

- Complement

- $a + a' = 1$
 - $a * a' = 0$

- Apply Boolean algebra:

$$f = c'hp + c'hp' + c'h'p$$

$$f = c'h(p + p') + c'h'p \text{ (by the distributive property)}$$

$$f = c'h(1) + c'h'p \text{ (by the complement property)}$$

$$f = c'h + c'h'p \text{ (by the identity property)}$$

$$f = hc' + h'pc' \text{ (by the commutative property)}$$

Same! Yes, we can use it.

a

Boolean Algebra:

Additional Properties

■ Null elements

➤ $a + 1 = 1$

➤ $a * 0 = 0$

■ Idempotent Law

➤ $a + a = a$

➤ $a * a = a$

■ Involution Law

➤ $(a')' = a$

■ DeMorgan's Law

➤ $(a + b)' = a'b'$


➤ $(ab)' = a' + b'$

➤ *Very useful!*

■ To prove, just evaluate all possibilities

Representations of Boolean Functions

2.6

 

■ A function can be represented in different ways

- Above shows seven representations of the same functions $F(a,b)$, using four different methods: English, Equation, Circuit, and Truth Table

Truth Table Representation of Boolean Functions

- Define value of F for each possible combination of input values

- 2-input function: 4 rows
- 3-input function: 8 rows
- 4-input function: 16 rows

- Q: Use truth table to define function $F(a,b,c)$ that is 1 when abc is 5 or greater in binary

a	b	F
0	0	
0	1	
1	0	
1	1	

(a)

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b)

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



a

a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	


(c)

Converting among Representations

  - Can convert from any representation to another
- Common conversions
 - Equation to circuit (we did this earlier)
 - Circuit to equation
 - Start at inputs, write expression of each gate output



Converting among Representations

 

More common conversions

- Truth table to equation (which we can then convert to circuit)
 - Easy—just OR each input term that should output 1
- Equation to truth table
 - Easy—just evaluate equation for each input combination (row)
 - Creating intermediate columns helps

Inputs		Outputs	Term
a	b	F	F = sum of
0	0	1	a'b'
0	1	1	a'b
1	0	0	
1	1	0	

$$F = a'b' + a'b$$

Q: Convert to equation

a	b	c	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	1	ab'c
1	1	0	1	abc'
1	1	1	1	abc

$$F = ab'c + abc' + abc$$

Q: Convert to truth table: $F = a'b' + a'b$

Inputs				Output
a	b	a'b'	a'b	F
0	0	1	0	1
0	1	0	1	1
1	0	0	0	0
1	1	0	0	0

Example: Converting from Truth Table to Equation

- Parity bit: Extra bit added to data, intended to enable detection of error (a bit changed unintentionally)
 - e.g., errors can occur on wires due to electrical interference
- Even parity: Set parity bit so total number of 1s (data + parity) is even
 - e.g., if data is 001, parity bit is 1 → 0011 has even number of 1s
- Want equation, but easiest to start from truth table for this example


a	b	c	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Convert to eqn.

$$P = a'b'c + a'bc' + ab'c' + abc$$

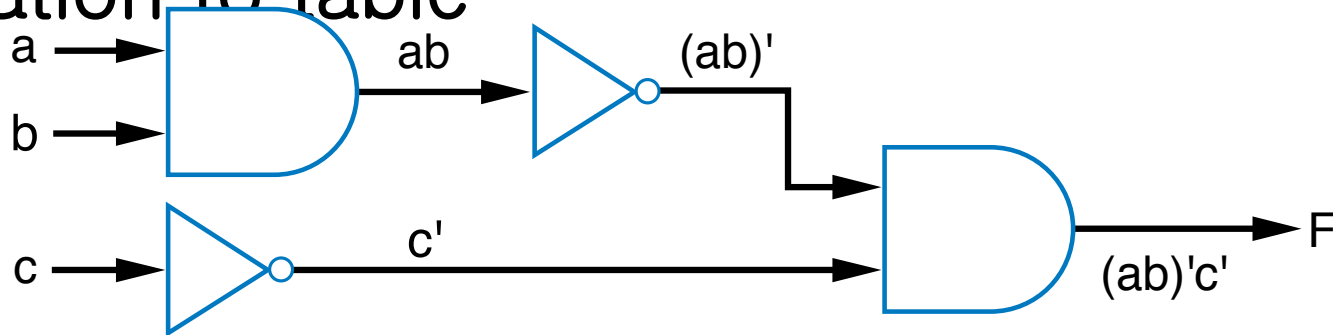Example: Converting from Circuit to Truth Table

- First convert to circuit to equation, then equation to table



Inputs						Outputs
a	b	c	ab	$(ab)'$	c'	F
0	0	0	0	1	1	1
0	0	1	0	1	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	1	0	1	0
1	1	1	1	0	0	0