

# Digital circuit design: combinational logic and optimization

# Contents

- Truth table
- Canonical form – sum of minterms
- Combinational logic design with examples
- K-map
- More gates and their properties
- Multiplexer and decoder

# Standard Representation: Truth Table

- How can we determine if two functions are the same?
  - Recall automatic door example
    - Same as  $f = hc' + h'pc'$ ?
    - Used algebraic methods
    - But if we failed, does that prove *not* equal? No.
- Solution: Convert to truth tables
  - Only ONE truth table representation of a given function
    - **Standard** representation—for given function, only one version in standard form exists

$$f = c'hp + c'hp' + c'h'$$

$$f = c'h(p + p') + c'h'p$$

$$f = c'h(1) + c'h'p$$

$$f = c'h + c'h'p$$

(what if we stopped here?)

$$f = hc' + h'pc'$$

Q: Determine if  $F = ab + a'$  is same function as  $F = a'b' + a'b + ab$ , by converting each to truth table first

$F = ab + a'$		
a	b	F
0	0	1
0	1	1
1	0	0
1	1	1

$F = a'b' + a'b + ab$		
a	b	F
0	0	1
0	1	1
1	0	0
1	1	1

Same

# Truth Table Canonical Form

- Q: Determine via truth tables whether  $ab + a'$  and  $(a+b)'$  are equivalent

$F = ab + a'$			$F = (a+b)'$		
a	b	F	a	b	F
0	0	1	0	0	1
0	1	1	0	1	0
1	0	0	1	0	0
1	1	1	1	1	0

Not equivalent

# Canonical Form – Sum of Minterms

- Truth tables too big for numerous inputs
- Use standard form of equation instead
  - Known as **canonical form**
  - Regular algebra: group terms of polynomial by power
    - $ax^2 + bx + c$  ( $3x^2 + 4x + 2x^2 + 3 + 1 \rightarrow 5x^2 + 4x + 4$ )
  - Boolean algebra: create sum of minterms
    - **Minterm**: product term with every function literal appearing exactly once, in true or complemented form
    - Just multiply-out equation until sum of product terms
    - Then expand each term until all terms are minterms

Q: Determine if  $F(a,b)=ab+a'$  is equivalent to  $F(a,b)=a'b'+a'b+ab$ , by converting first equation to canonical form (second already is)

$F = ab+a'$  (already sum of products)

$F = ab + a'(b+b')$  (expanding term)

$F = ab + a'b + a'b'$  (Equivalent – same three terms as other equation)

# Canonical Form – Sum of Minterms

- Q: Determine whether the functions  $G(a,b,c,d,e) = abcd + a'bcde$  and  $H(a,b,c,d,e) = abcde + abcde' + a'bcde + a'bcde(a' + c)$  are equivalent.

$$G = abcd + a'bcde$$

$$G = abcd(e+e') + a'bcde$$

$$G = abcde + abcde' + a'bcde$$

$$G = a'bcde + abcde' + abcde \quad (\text{sum of minterms form})$$

Equivalent

$$H = abcde + abcde' + a'bcde + a'bcde(a' + c)$$

$$H = abcde + abcde' + a'bcde + a'bcdea' + a'bcdec$$

$$H = abcde + abcde' + a'bcde + a'bcde + a'bcde$$

$$H = abcde + abcde' + a'bcde$$


$$H = a'bcde + abcde' + abcde$$

# Compact Sum of Minterms Representation


- List each minterm as a number
- Number determined from the binary representation of its variables' values
  - $a'bcde$  corresponds to 01111, or 15
  - $abcde'$  corresponds to 11110, or 30
  - $abcde$  corresponds to 11111, or 31
- Thus,  $H = a'bcde + abcde' + abcde$  can be written as:
  - $H = \sum m(15, 30, 31)$
  - "H is the sum of minterms 15, 30, and 31"

# Multiple-Output Circuits

- Many circuits have more than one output
- Can give each a separate circuit, or can share gates
- Ex:  $F = \underline{ab} + c'$ ,  $G = \underline{ab} + bc$

 



Option 1: Separate circuits

 

Option 2: Shared gates



 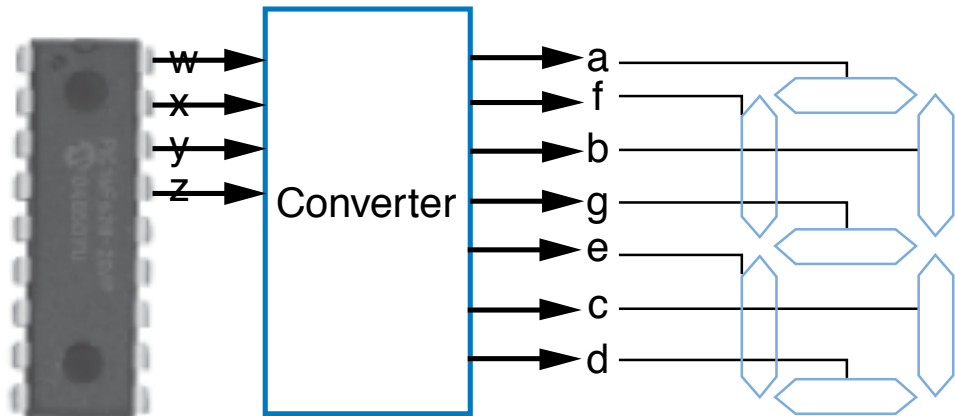
# Multiple-Output Example: BCD to 7-Segment Converter



# Multiple-Output Example: BCD to 7-Segment Converter

TABLE 2-4 4-bit binary number to seven-segment display truth table

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

 

$$a = w'x'y'z' + w'x'yz' + w'x'yz + w'xy'z + w'xyz' + w'xyz + wx'y'z' + wx'y'z$$

$$b = w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz + w'xy'z' + w'xyz + wx'y'z' + wx'y'z$$

...

# Combinational Logic Design Process

Step	Description
Step 1: Capture behavior <b>Capture</b> the function	Create a truth table or equations, <i><b>whichever is most natural for the given problem</b></i> , to describe the desired behavior of each output of the combinational logic.
Step 2: Convert to circuit 2A: <b>Create</b> equations 2B: <b>Implement</b> as a gate-based circuit	<p>This substep is only necessary if you captured the function using a truth table instead of equations. Create an equation for each output by ORing all the minterms for that output. Simplify the equations if desired.</p> <p>For each output, create a circuit corresponding to the output's equation. (Sharing gates among multiple outputs is OK optionally.)</p>

# Example: Three 1s Pattern Detector

- Problem: Detect three consecutive 1s in 8-bit input: abcdefgh

- 00011101 → 1
- 10101011 → 0
- 11110000 → 1


- **Step 1: Capture** the function

- Truth table or equation?
  - Truth table too big:  $2^8=256$  rows
  - Equation: create terms for each possible case of three consecutive 1s

- $y = abc + bcd + cde + def + efg + fgh$

- **Step 2a: Create** equation -- already done

 - **Step 2b: Implement** as a gate-based circuit



# Example: Number of 1s Counter

- Problem: Output in binary on two outputs yz the # of 1s on three inputs

- $010 \rightarrow 01$
- $101 \rightarrow 10$
- $000 \rightarrow 00$

– **Step 1: Capture** the function

- Truth table or equation?
  - Truth table is straightforward


– **Step 2a: Create** equations

- $y = a'bc + ab'c + abc' + abc$
- $z = a'b'c + a'bc' + ab'c' + abc$
- Optional: Let's simplify y:

–  $y = a'bc + ab'c + ab(c' + c) = a'bc + ab'c + ab$


– **Step 2b: Implement** as a gate-based circuit

Inputs			# of 1s	Outputs	
a	b	c		y	z
0	0	0	(0)	0	0
0	0	1	(1)	0	1
0	1	0	(1)	0	1
0	1	1	(2)	1	0
1	0	0	(1)	0	1
1	0	1	(2)	1	0
1	1	0	(2)	1	0
1	1	1	(3)	1	1

 


# Simplifying Notations

- Used in previous circuit

 

 
List inputs multiple times  
→ Less wiring in drawing



Draw inversion bubble  
rather than inverter. Or list  
input as complemented.
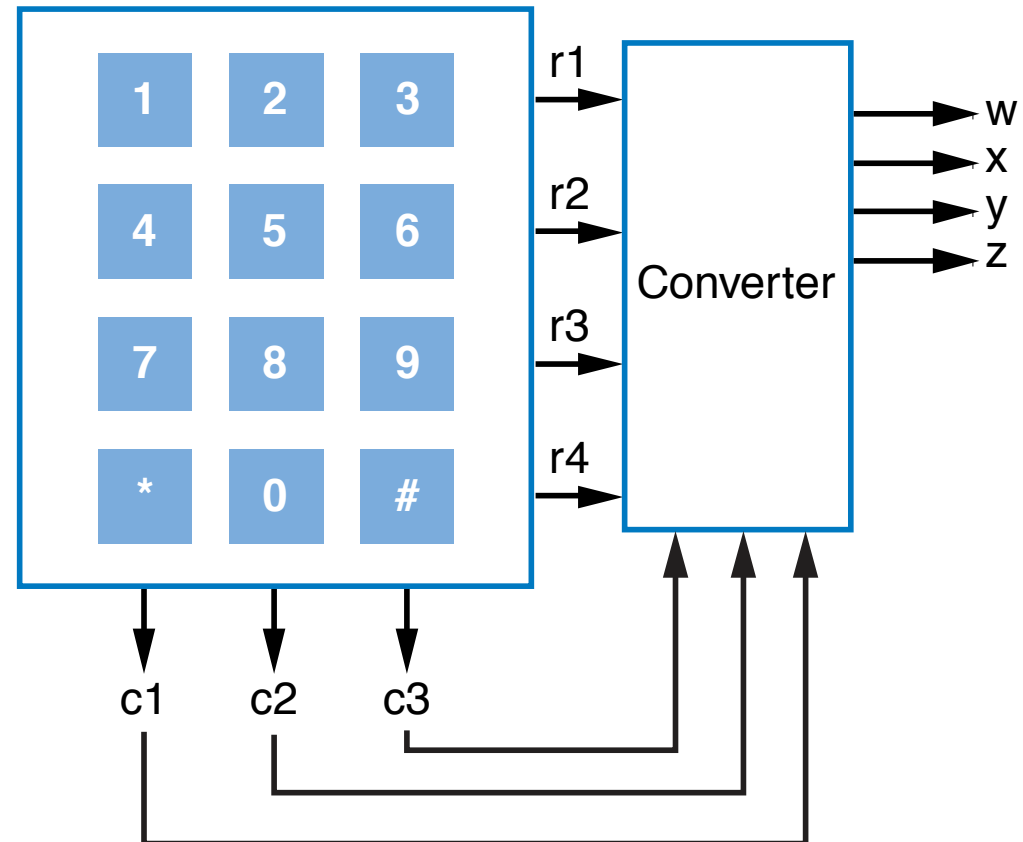
# Example: Keypad Converter

- Keypad has 7 outputs
  - One per row
  - One per column
- Key press sets one row and one column output to 1
  - Press "5" → r2=1, c2=1
- Goal: Convert keypad outputs into 4-bit binary number
  - 0-9 → 0000 to 1001
  - \* → 1010, # → 1011
  - nothing pressed: 1111



# Example: Keypad Converter

- Step 1: Capture behavior
  - Truth table too big ( $2^7$  rows); equations not clear either
  - Informal table can help

TABLE 2.7 Informal table for the 12-button keypad to 4-bit code converter.

Button	Signals	4-bit code outputs			
		w	x	y	z
1	r1 c1	0	0	0	1
2	r1 c2	0	0	1	0
3	r1 c3	0	0	1	1
4	r2 c1	0	1	0	0
5	r2 c2	0	1	0	1
6	r2 c3	0	1	1	0
7	r3 c1	0	1	1	1

Button	Signals	4-bit code outputs			
		w	x	y	z
8	r3 c2	1	0	0	0
9	r3 c3	1	0	0	1
*	r4 c1	1	0	1	0
0	r4 c2	0	0	0	0
#	r4 c3	1	0	1	1
(none)		1	1	1	1

Step 2b: Implement<sup>a</sup>  
as circuit (note  
sharable gates) ...

$$w = r3c2 + r3c3 + r4c1 + r4c3 + r1'r2'r3'r4'c1'c2'c3'$$

$$x = r2c1 + r2c2 + r2c3 + r3c1 + r1'r2'r3'r4'c1'c2'c3'$$

$$y = r1c2 + r1c3 + r2c3 + r3c1 + r4c1 + r4c3 + r1'r2'r3'r4'c1'c2'c3'$$


$$z = r1c1 + r1c3 + r2c2 + r3c1 + r3c3 + r4c3 + r1'r2'r3'r4'c1'c2'c3'$$

<sup>a</sup>


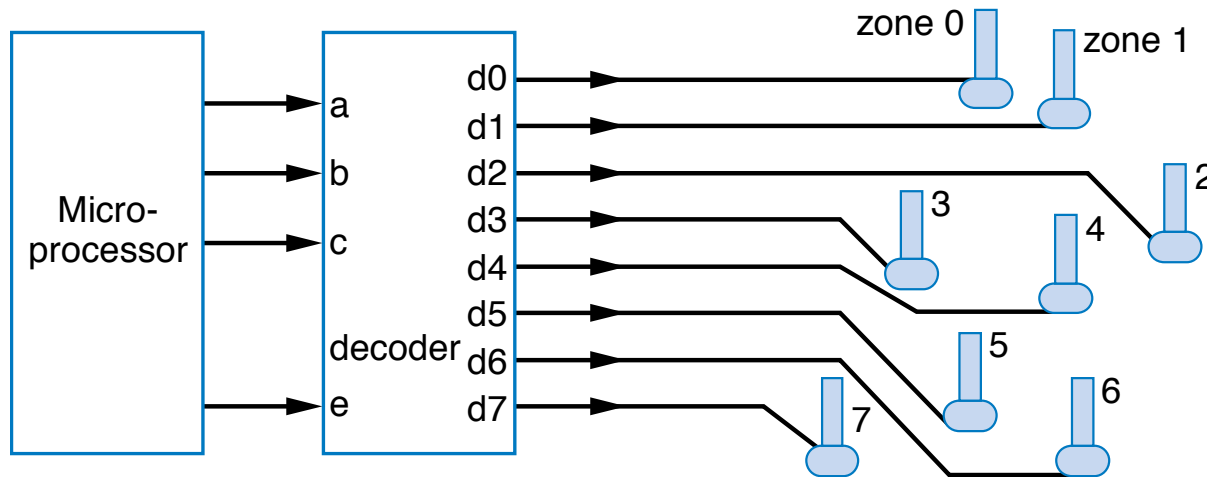
# Example: Sprinkler Controller

- Microprocessor outputs which zone to water (e.g., cba=110 means zone 6) and enables watering (e=1)
- Decoder should set appropriate valve to 1



Step 1: Capture behavior

$$d0 = a'b'c'e$$

$$d1 = a'b'ce$$

$$d2 = a'bc'e$$

$$d3 = a'bce$$

$$d4 = ab'c'e$$

$$d5 = ab'ce$$


$$d6 = abc'e$$

$$d7 = abc'e$$

*Equations seem like  
a natural fit*

# Example: Sprinkler Controller

- Step 2b: Implement as circuit

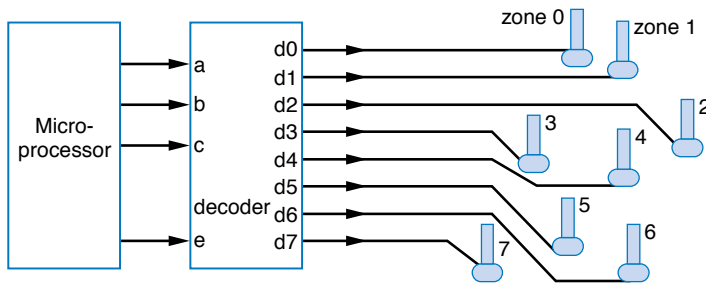

$$d0 = a'b'c'e$$

$$d1 = a'b'ce$$

$$d2 = a'bc'e$$


$$d3 = a'bce$$

$$d4 = ab'c'e$$



$$d5 = ab'ce$$

$$d6 = abc'e$$

$$d7 = abce$$

 

# More Gates

  


- NAND: Opposite of AND (“NOT AND”)
- NOR: Opposite of OR (“NOT OR”)
- XOR: Exactly 1 input is 1, for 2-input XOR. (For more inputs -- odd number of 1s)
- XNOR: Opposite of XOR (“NOT XOR”)
- NAND same as AND with power & ground switched
  - nMOS conducts 0s well, but not 1s (reasons beyond our scope) – so NAND is more efficient
- Likewise, NOR same as OR with power/ground switched
- NAND/NOR more common
- AND in CMOS: NAND with NOT
- OR in CMOS: NOR with NOT

# More Gates: Example Uses


- Aircraft lavatory sign example

- $S = (abc)'$

 


- Detecting all 0s

- Use NOR

 

- Detecting equality

- Use XNOR

 


- Detecting odd # of 1s

- Use XOR
  - Useful for generating “parity” bit common for detecting errors
 
# Completeness of NAND

- Any Boolean function can be implemented *using just NAND gates*. Why?
  - Need AND, OR, and NOT
  - NOT: 1-input NAND (or 2-input NAND with inputs tied together)
  - AND: NAND followed by NOT
  - OR: NAND preceded by NOTs
  - Thus, NAND is a universal gate
    - Can implement any circuit using just NAND gates
- Likewise for NOR



# Number of Possible Boolean Functions

- How many possible functions of 2 variables?

- $2^2$  rows in truth table, 2 choices for each
- $2^{(2^2)} = 2^4 = 16$  possible functions

- N variables

- $2^N$  rows
- $2^{(2^N)}$  possible functions





a	b	F
0	0	0 or 1 2 choices
0	1	0 or 1 2 choices
1	0	0 or 1 2 choices
1	1	0 or 1 2 choices

$2^4 = 16$   
possible functions

a	b	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		0	a AND b			a	b		a XOR b	a OR b	a NOR b	a XNOR b	b'	a'		a NAND b	1
    
# Decoders and Muxes

- **Decoder:** Popular combinational logic building block, in addition to logic gates
  - Converts input binary number to one high output
- 2-input decoder: four possible input binary numbers
  - So has four outputs, one for each possible input binary number
- Internal design
  - AND gate for each output to detect input combination
- Decoder with enable  $e$ 
  - Outputs all 0 if  $e=0$
  - Regular behavior if  $e=1$
- $n$ -input decoder:  $2^n$  outputs



# Decoder Example

- New Year's Eve Countdown Display
  - Microprocessor counts from 59 down to 0 in binary on 6-bit output
  - Want illuminate one of 60 lights for each binary number
  - Use 6x64 decoder
    - 4 outputs unused

