
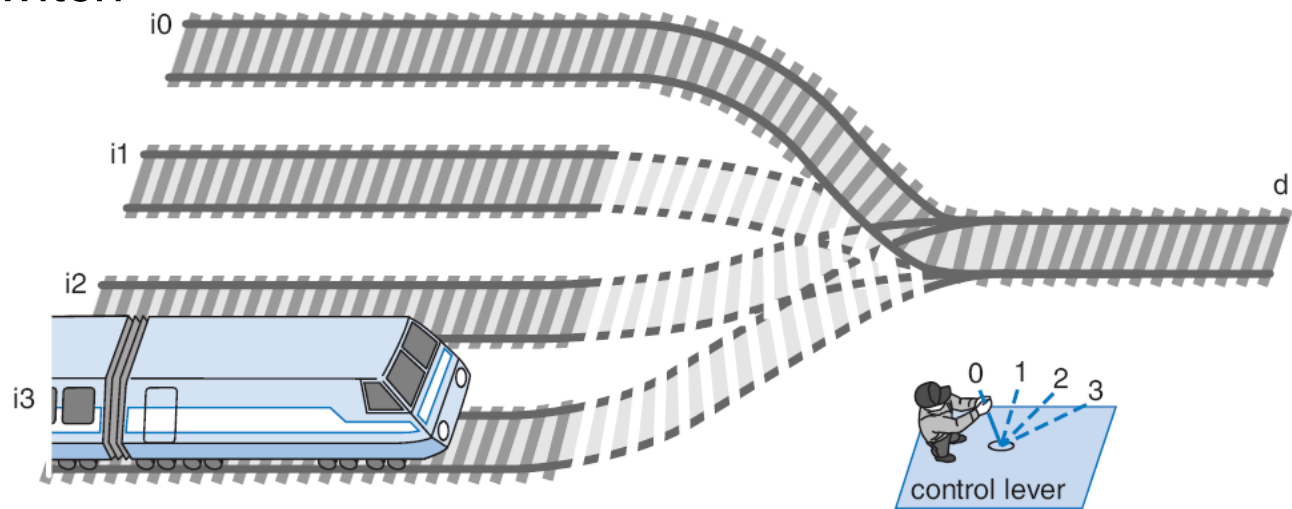


Multiplexor (Mux)


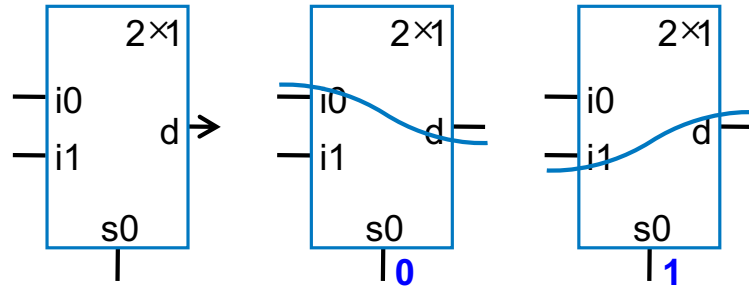
- Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
 - 4 input mux \rightarrow needs 2 select inputs to indicate which input to route through
 - 8 input mux \rightarrow 3 select inputs
 - N inputs $\rightarrow \log_2(N)$ selects
 - Like a rail yard switch




Mux Internal Design



2x1 mux

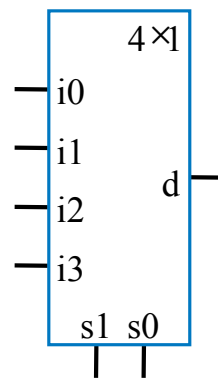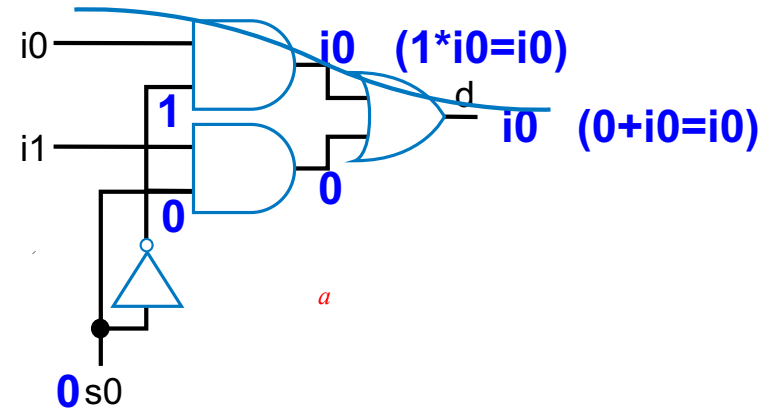


4x1 mux

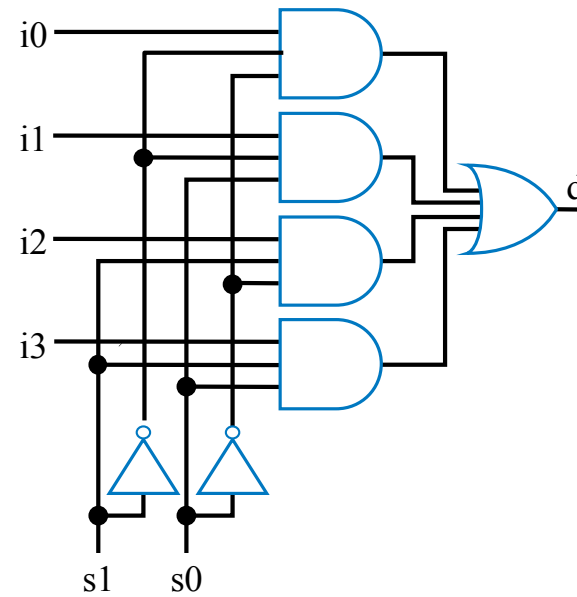


Mux Example

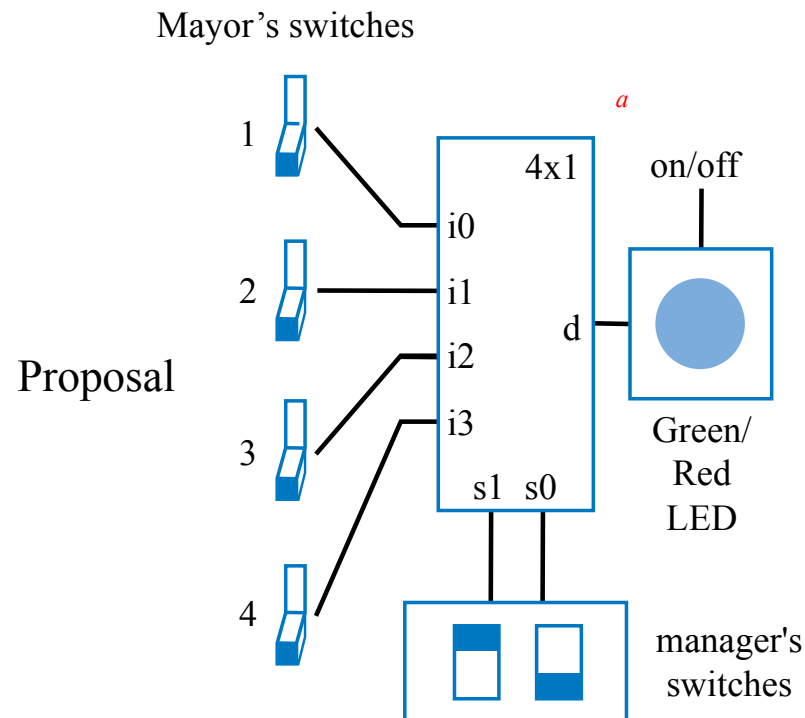- City mayor can set four switches up or down, representing his/her vote on each of four proposals, numbered 0, 1, 2, 3
- City manager can display any such vote on large green/red LED (light) by setting two switches to represent binary 0, 1, 2, or 3
- Use 4x1 mux




Muxes Commonly Together – N-bit Mux

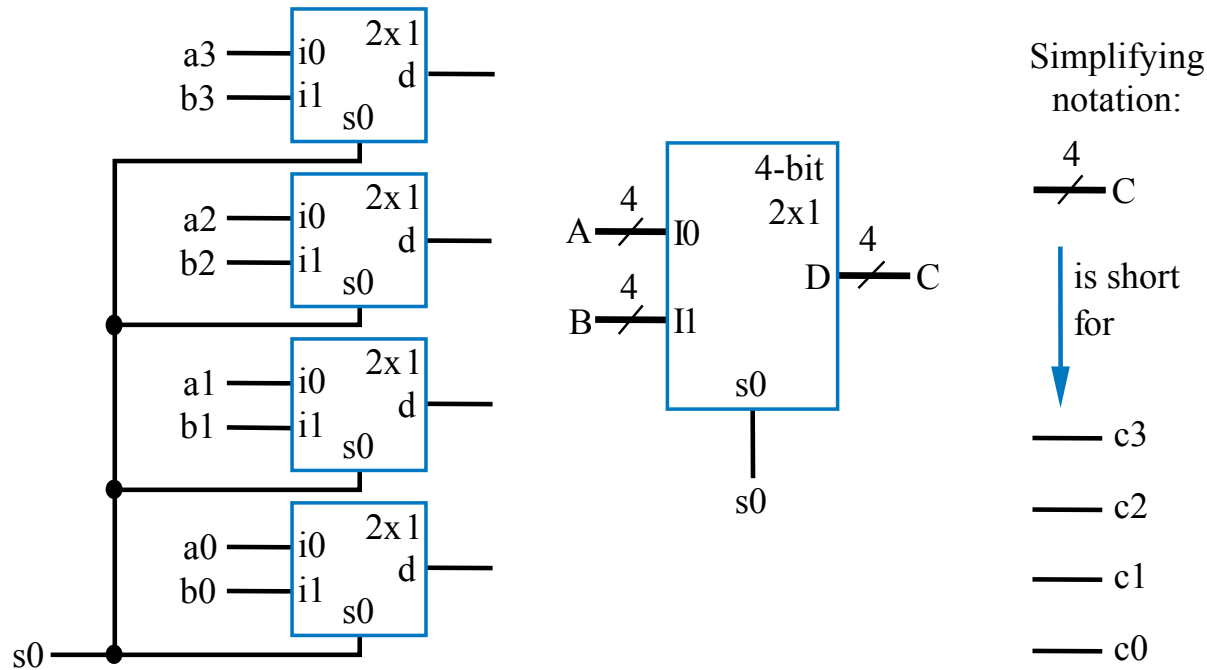

- Ex: Two 4-bit inputs, A ($a3$ $a2$ $a1$ $a0$), and B ($b3$ $b2$ $b1$ $b0$)
 - 4-bit 2x1 mux (just four 2x1 muxes sharing a select line) can select between A or B


N-bit Mux Example

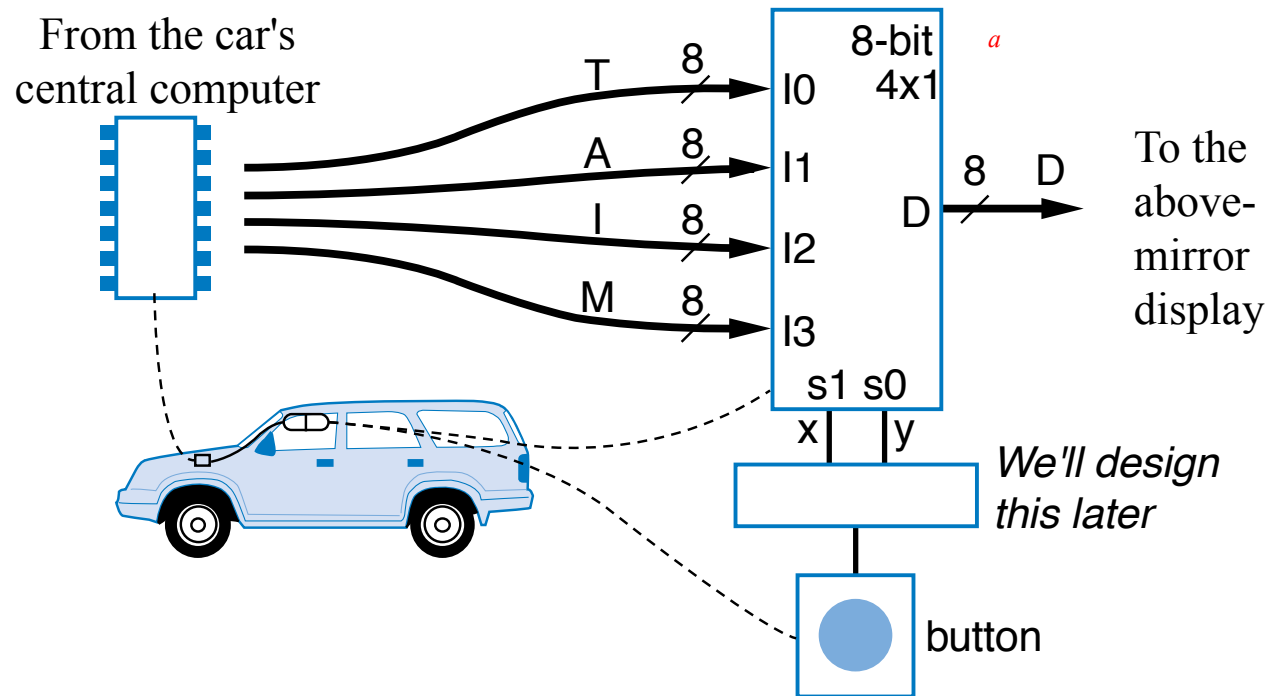

- Four possible display items
 - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) – each is 8-bits wide
 - Choose which to display on D using two inputs x and y
 - Pushing button sequences to the next item
 - Use 8-bit 4x1 mux


Additional Considerations

Non-Ideal Gate Behavior -- Delay

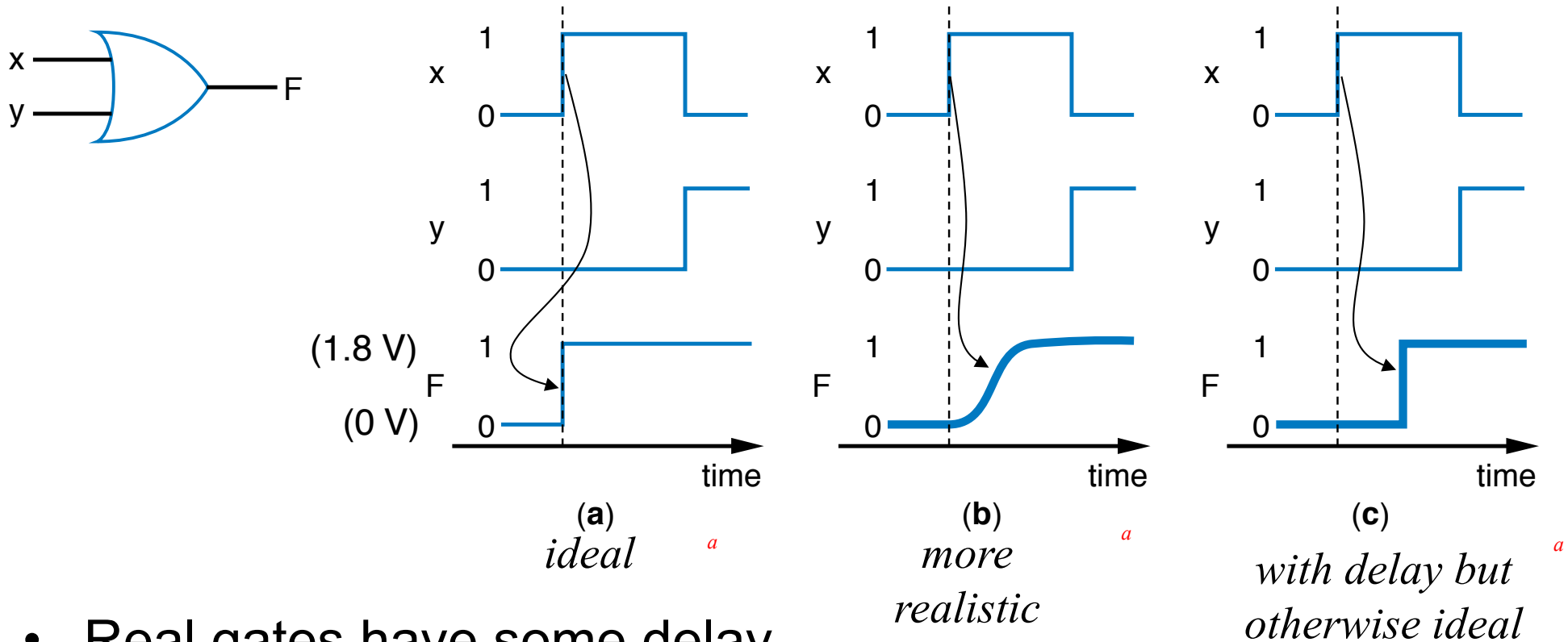

- Real gates have some delay
 - Outputs don't change immediately after inputs change


Circuit Delay and Critical Path

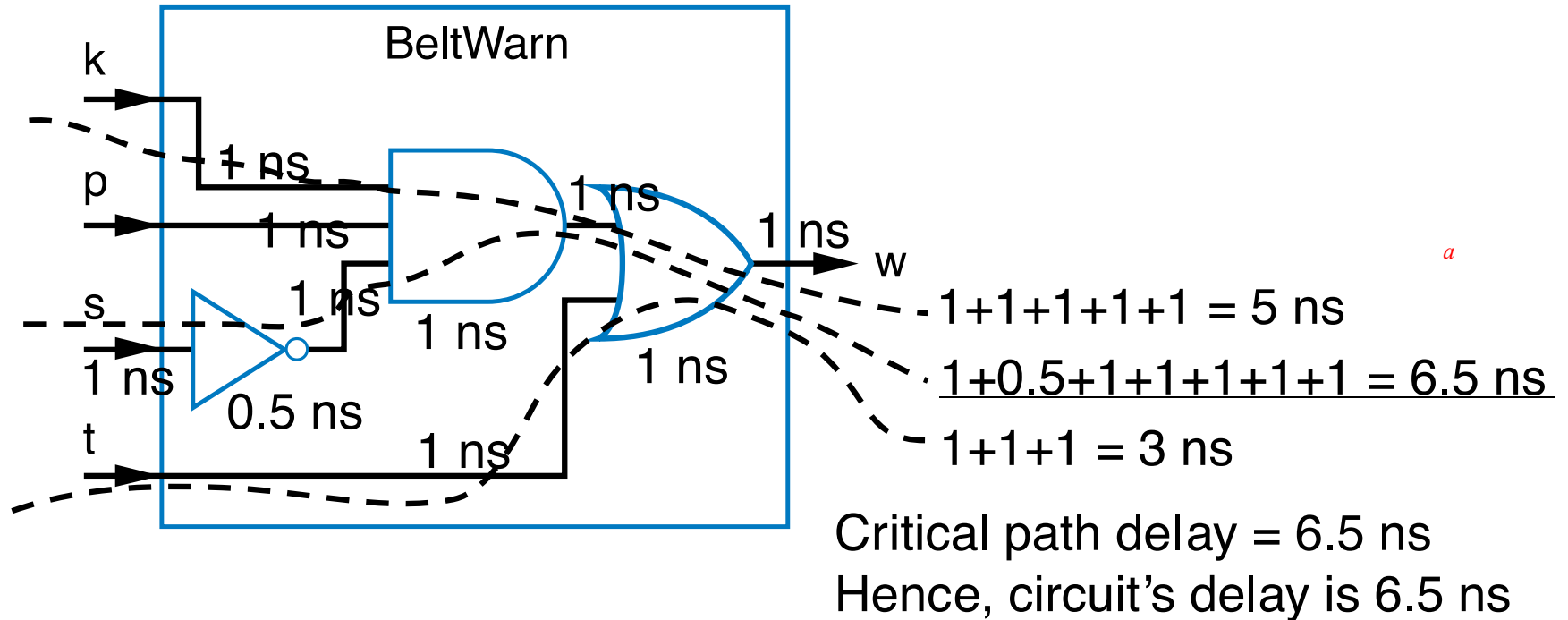




- Wires also have delay
- Assume gates and wires have delays as shown
- Path delay – time for input to affect output
- Critical path – path with longest path delay
- Circuit delay – delay of critical path

Active Low Inputs

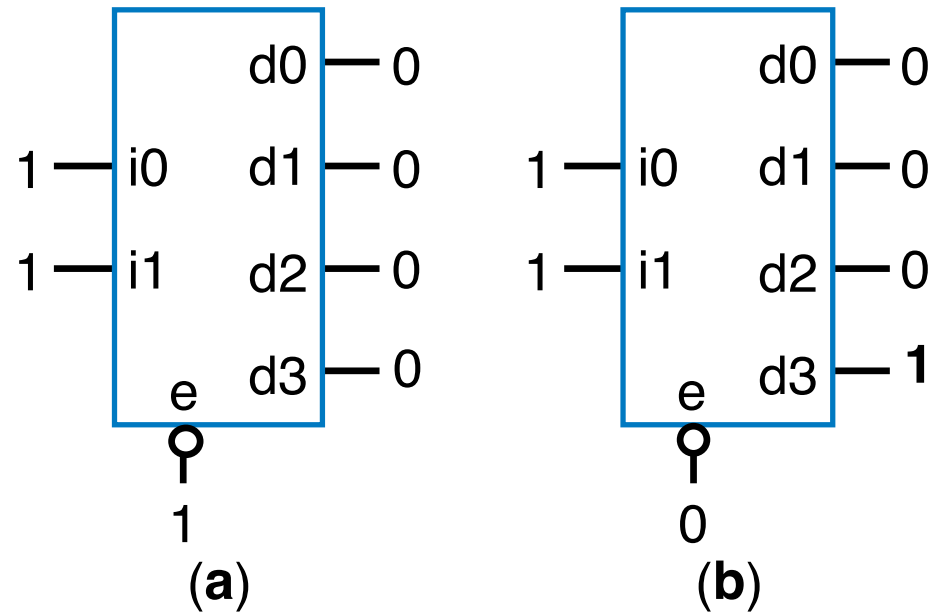- Data inputs: flow through component (e.g., mux data input)
- Control input: influence component behavior
 - Normally active high – 1 causes input to carry out its purpose
 - Active low – Instead, 0 causes input to carry out its purpose
 - Example: 2x4 decoder with active low enable
 - 1 disables decoder, 0 enables
 - Drawn using inversion bubble



Schematic Capture and Simulation

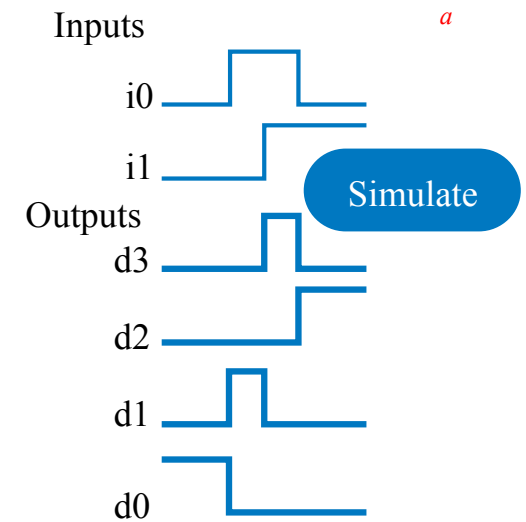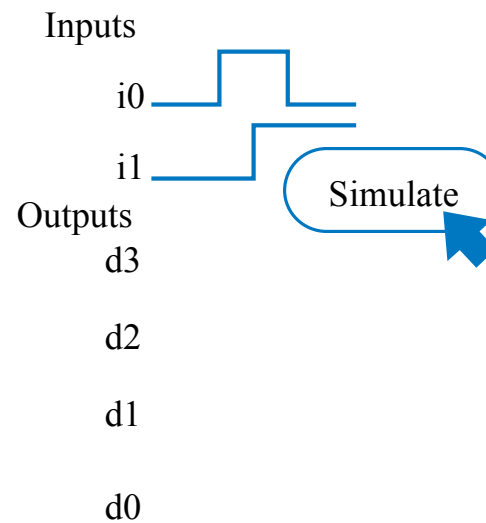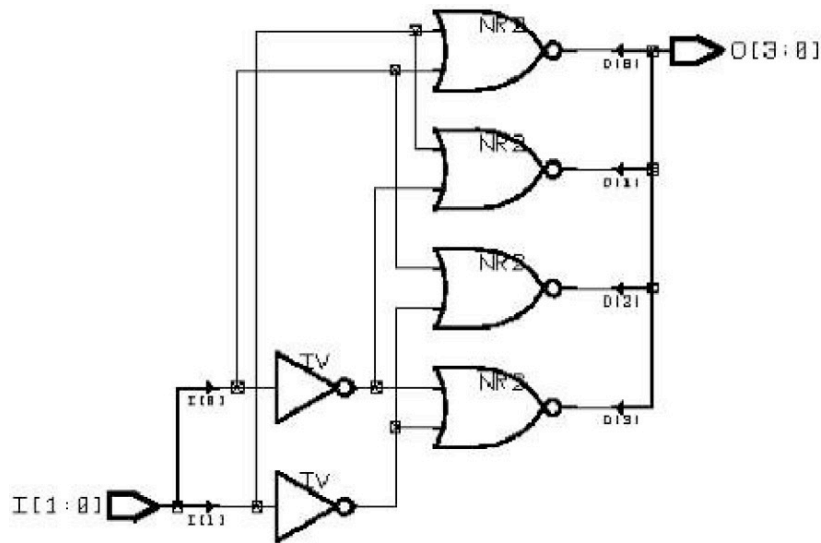

- **Schematic capture**
 - Computer tool for user to capture logic circuit graphically
- **Simulator**
 - Computer tool to show what circuit outputs would be for given inputs
 - Outputs commonly displayed as **waveform**

Appendix: Boolean properties and examples

Boolean Algebra Properties


- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - Can write as: $a(b+c) = ab + ac$
 - $a + (b * c) = (a + b) * (a + c)$
 - (This second one is tricky!)
 - Can write as: $a+(bc) = (ab)(ac)$
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- To prove, just evaluate all possibilities

Example uses of the properties

- Show abc' equivalent to $c'ba$.
 - Use commutative property:
 - $a*b*c' = a*c'*b = c'*a*b = c'*b*a$
- Show $abc + abc' = ab$.
 - Use first distributive property
 - $abc + abc' = ab(c+c')$
 - Complement property
 - Replace $c+c'$ by 1: $ab(c+c') = ab(1)$.
 - Identity property
 - $ab(1) = ab*1 = ab$.
- Show $x + x'z$ equivalent to $x + z$.
 - Second distributive property
 - Replace $x+x'z$ by $(x+x')*(x+z)$.
 - Complement property
 - Replace $(x+x')$ by 1,
 - Identity property
 - replace $1*(x+z)$ by $x+z$.

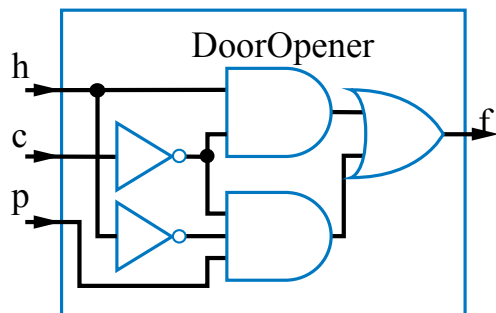Example that Applies Boolean Algebra Properties

- Want automatic door opener circuit (e.g., for grocery store)
 - Output: $f=1$ opens door
 - Inputs:
 - $p=1$: person detected
 - $h=1$: switch forcing hold open
 - $c=1$: key forcing closed
 - Want open door when
 - $h=1$ and $c=0$, or
 - $h=0$ and $p=1$ and $c=0$
 - Equation: $f = hc' + h'pc'$



- Can the circuit be simplified?

$$f = hc' + h'pc'$$


$$f = c'h + c'h'p \quad (\text{by the commutative property})$$

$$f = c'(h + h'p) \quad (\text{by the first distrib. property})$$

$$f = c'((h+h')*(h+p)) \quad (\text{2nd distrib. prop.; tricky one})$$

$$f = c'((1)*(h+p)) \quad (\text{by the complement property})$$
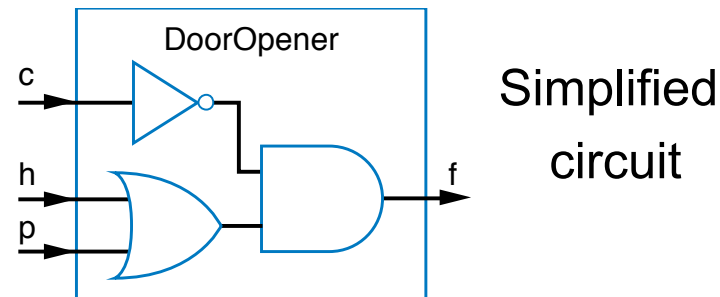
$$f = c'(h+p) \quad (\text{by the identity property})$$




Simplification of circuits is covered ₃₈
in Sec. 2.11 / Sec 6.2.

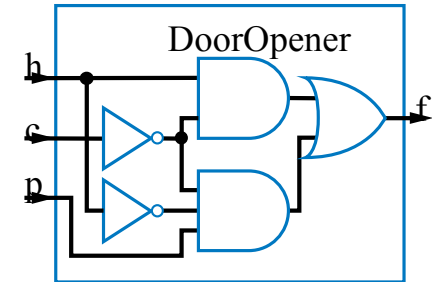Example that Applies Boolean Algebra Properties



- Found inexpensive chip that computes:
 - $f = c'hp + c'hp' + c'h'p$
 - Can we use it for the door opener?
 - Is it the same as $f = hc' + h'pc'$?
- Apply Boolean algebra:
 - Commutative
 - $a + b = b + a$
 - $a * b = b * a$
 - Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
 - Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
 - Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
 - Complement
 - $a + a' = 1$
 - $a * a' = 0$



$$f = c'hp + c'hp' + c'h'p$$

$$f = c'h(p + p') + c'h'p \text{ (by the distributive property)}$$

$$f = c'h(1) + c'h'p \text{ (by the complement property)}$$

$$f = c'h + c'h'p \text{ (by the identity property)}$$

$$f = hc' + h'pc' \text{ (by the commutative property)}$$

Same! Yes, we can use it.

Boolean Algebra: Additional Properties

- Null elements
 - $a + 1 = 1$
 - $a * 0 = 0$
- Idempotent Law
 - $a + a = a$
 - $a * a = a$
- Involution Law
 - $(a')' = a$
- DeMorgan's Law
 - $(a + b)' = a'b'$
 - $(ab)' = a' + b'$
 - *Very useful!*
- To prove, just evaluate all possibilities



Example Applying DeMorgan's Law

$$(a + b)' = a'b'$$
$$(ab)' = a' + b'$$

Aircraft lavatory sign example



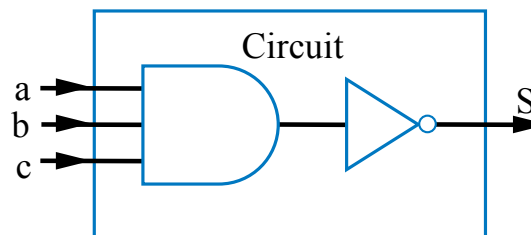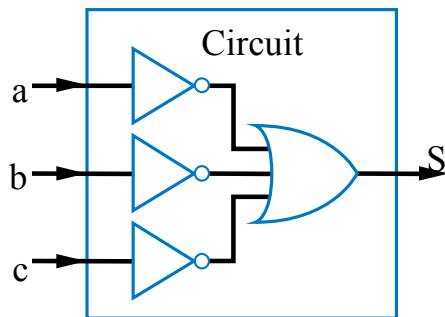- Behavior
 - Three lavatories, each with sensor (a, b, c), equals 1 if door locked
 - Light “Available” sign (S) if any lavatory available
- Equation and circuit
 - $S = a' + b' + c'$
- Transform
 - $(abc)' = a' + b' + c'$ (by DeMorgan's Law)
 - $S = (abc)'$
- New circuit



- Alternative: Instead of lighting “Available,” light “Occupied”
- Opposite of “Available” function
 - $S = a' + b' + c'$
- So $S' = (a' + b' + c')'$
 - $S' = (a')' * (b')' * (c')'$ (by DeMorgan's Law)
 - $S' = a * b * c$ (by Involution Law)
- Makes intuitive sense
 - Occupied if all doors are locked

Example Applying Properties

- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- Null elements
 - $a + 1 = 1$
 - $a * 0 = 0$
- Idempotent Law
 - $a + a = a$
 - $a * a = a$
- Involution Law
 - $(a')' = a$
- DeMorgan's Law
 - $(a + b)' = a'b'$
 - $(ab)' = a' + b'$
- For door opener $f = c'(h+p)$, *prove* door stays closed ($f=0$) when $c=1$
 - $f = c'(h+p)$
 - *Let $c = 1$* (door forced closed)
 - $f = 1'(h+p)$
 - $f = 0(h+p)$
 - $f = 0h + 0p$ (by the distributive property)
 - $f = 0 + 0$ (by the null elements property)
 - $f = 0$

Complement of a Function

- Commonly want to find complement (inverse) of function F
 - 0 when F is 1; 1 when F is 0
- Use DeMorgan's Law repeatedly
 - Note: DeMorgan's Law defined for more than two variables, e.g.:
 - $(a + b + c)' = (abc)'$
 - $(abc)' = (a' + b' + c')$
- Complement of $f = w'xy + wx'y'z'$
 - $f' = (w'xy + wx'y'z')'$
 - $f' = (w'xy)'(wx'y'z')'$ (by DeMorgan's Law)
 - $f' = (w+x'+y')(w'+x+y+z)$ (by DeMorgan's Law)
- Can then expand into sum-of-products form